

Modern Current Source Inverter Drives: Modulation, Control, Topologies

Power Electronics for Energy Transition Symposium @SAL

Spasoje Mirić et al.



University of Innsbruck, Institute for Mechatronics
Innsbruck Drives and Energy Systems Laboratory (iDES)
Technikerstraße 13a, Floor 1, Office 128
<https://www.uibk.ac.at/mechatronik/ides/>

September 30, 2025



Modern Current Source Inverter Drives: Modulation, Control, Topologies

Power Electronics for Energy Transition Symposium @SAL

S. Mirić | P. Pejović | T. Ohno | M. Haider



University of Innsbruck, Institute for Mechatronics
Innsbruck Drives and Energy Systems Laboratory (iDES)
Technikerstraße 13a, Floor 1, Office 128
<https://www.uibk.ac.at/mechatronik/ides/>






September 30, 2025





Introduction: VSI and CSI for Drive Systems

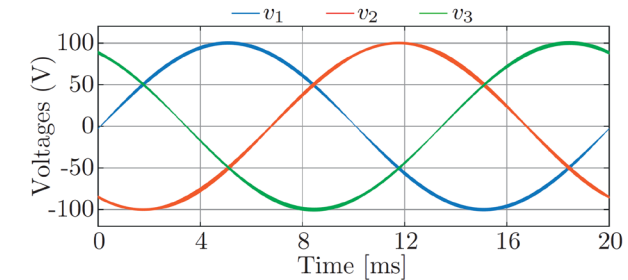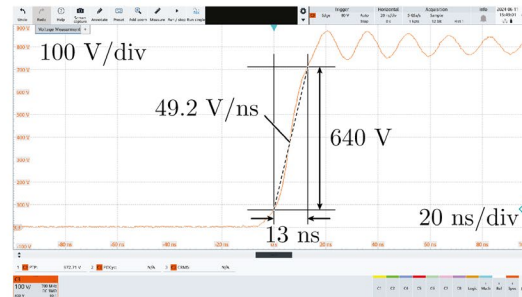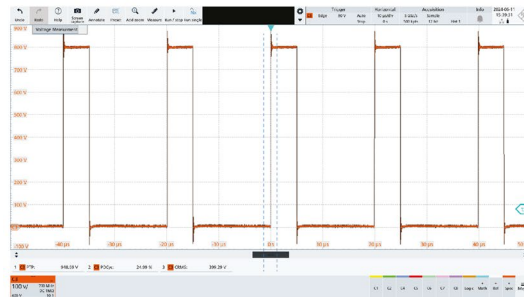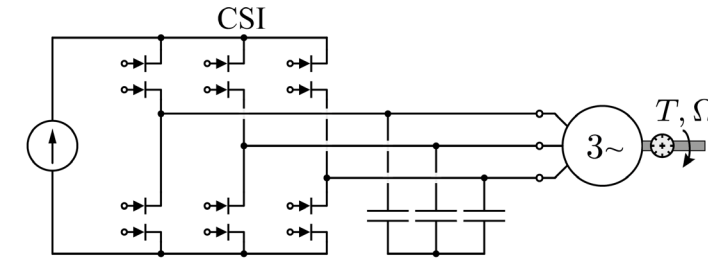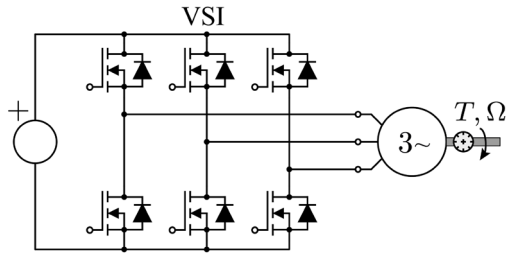
- Voltage Source Inverter (VSI) drive system → typically direct connection of the motor terminals to the switch node
- VSI generates pulsed voltage over motor windings → interturn overvoltage / harmonic losses / bearing currents / EMI / insulation aging



- Current Source Inverter (CSI) drive system → provides 'smooth' line voltages over the motor windings due to output filter capacitors
- Therefore, CSI 'could' potentially solve high-frequency issues typical for the VSI drive systems
- Blocking of voltage and current in both directions for CSI → Monolithic Bidirectional Power Transistors

Introduction: Modulation VSI and CSI?

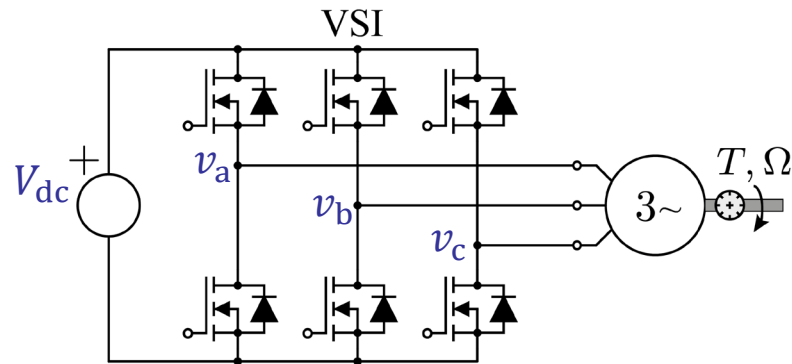
- Pulse width modulation (PWM) is well established and mainly used for VSIs
- Duty cycles are calculated directly from the voltage reference



$$d_a = \frac{\langle v_a \rangle}{V_{dc}} \quad d_b = \frac{\langle v_b \rangle}{V_{dc}} \quad d_c = \frac{\langle v_c \rangle}{V_{dc}}$$

- PWM for VSIs is done per half-bridge
- For more than 3 phases, the same principle applies: voltage reference divide by the DC link voltage
- To get more voltage amplitude → zero voltage component

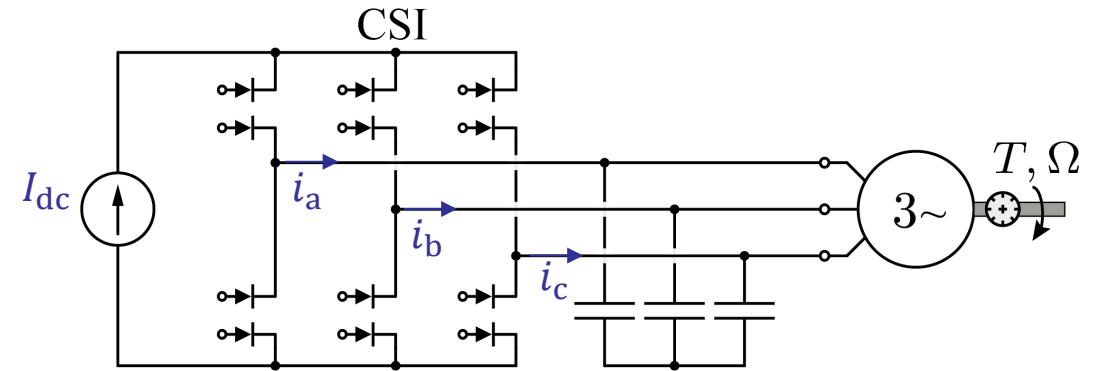- For CSIs the best established modulation method is SVM
- There are some PWM approaches for CSI, but it is not so straightforward like with VSIs



~~$$d_a = \frac{i_a}{I_{dc}} \quad d_b = \frac{i_b}{I_{dc}} \quad d_c = \frac{i_c}{I_{dc}}$$~~

- Duty cycles for CSI can not be calculated directly from the current reference like for VSIs, or can they?
- There is no general modulation method for CSIs that works for any number of phases, is there a way to do it?






Content

- ▶ PWM Method for CSIs with Arbitrary Number of Phases
- ▶ uniCSI: CSI Topology for Variable Reluctance Machines
- ▶ Equivalent DC Machine (E-DCM) Concept
 - Permanent Magnet Synchronous Machines (PMSMs)
 - Variable Reluctance Machines (VRM)
- ▶ Conclusions

CSI Commutation: per Cell

- Current source inverter modulation process is not straightforward as for the voltage source inverters (VSIs)
- For VSIs, duty cycles can be calculated by simply dividing the desired voltage per phase with the DC link voltage
- For CSIs, such direct approach as for VSIs is not possible since we have to actually always ensure the ‘flow’ of DC link current
- For CSIs there has to be always one and only one of the upper switches on, and one and only one of the lower switches on

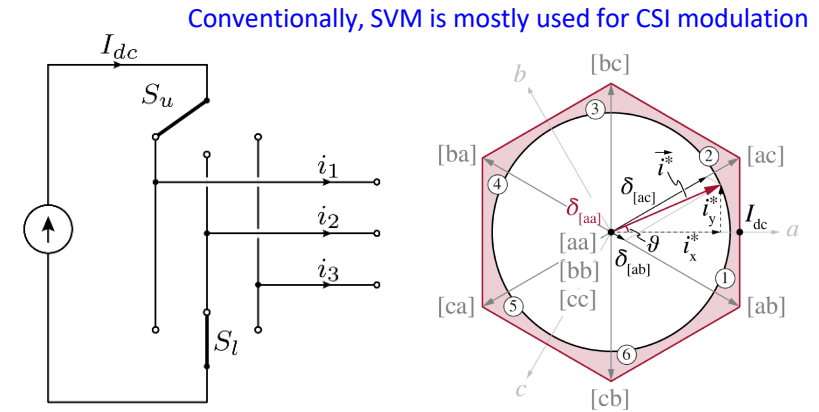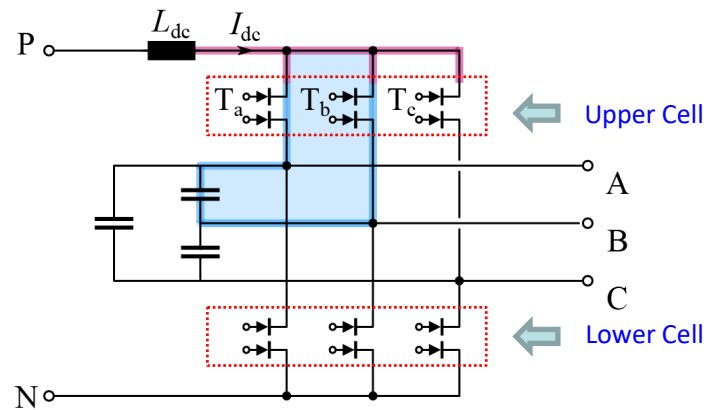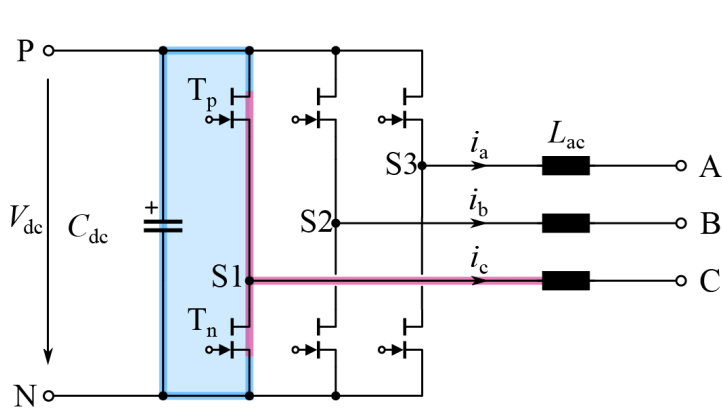



- VSI commutation loop → half bridge
- CSI commutation loop → cell

Picture source: Nain, N., Kovacevic-Badstuebner, I., Huber, J., Grossner, U., & Kolar, J. W. (2022, October). Design aspects of three-phase current-source converter commutation cells with monolithic bidirectional GaN transistors. In 2022 IEEE Energy Conversion Congress and Exposition (ECCE) (pp. 1-8). IEEE.



CSI Modulation: Requirements

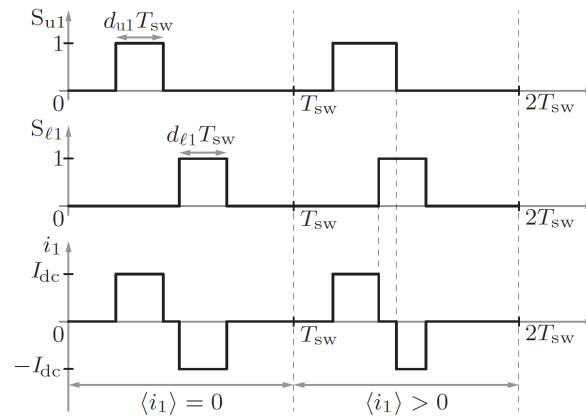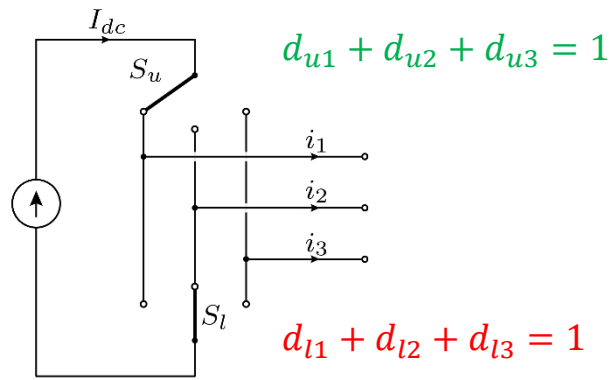- The task of the modulation is to ensure the desired value of the average phase current at the output
- Upper switch on → positive current pulse; lower switch on → negative current pulse; both switches on → zero current
- Every switching state must ensure the 'flow' of the DC link current



Average value of the current $\langle i_1 \rangle$ is obtained by averaging the DC link current pulses.

$$\langle i_1 \rangle = I_{dc}(d_{u1} - d_{l1})$$

- Current source inverter modulation process has to ensure the following two conditions:

1. Average value of the phase current: $\langle i_1 \rangle = I_{dc}(d_{u1} - d_{l1})$
2. Continuity of the DC link current: $d_{u1} + d_{u2} + d_{u3} = 1$ and $d_{l1} + d_{l2} + d_{l3} = 1$




CSI Modulation: 1st Requirement – Phase Current Average Value

- CSI needs to provide to the AC load desired averaged phase current value $\langle i_1 \rangle$
- The phase current is ‘algebraically’ obtained from the duty cycles and the DC link current value, and it is equal to the difference of the upper and lower duty cycles:

$$\langle i_1 \rangle = I_{dc}(d_{u1} - d_{l1})$$

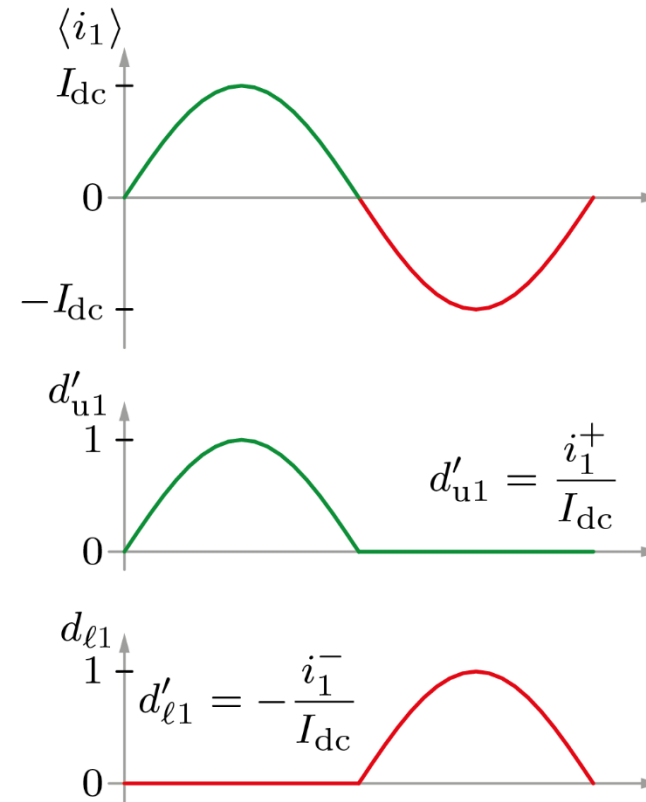- We can have an extremely simple approach to obtain the phase current:
 - for $\langle i_1 \rangle > 0 \rightarrow$ put $d'_{l1} = 0$
 - for $\langle i_1 \rangle < 0 \rightarrow$ put $d'_{u1} = 0$






$$\langle i_1 \rangle = I_{dc}(d'_{u1} - d'_{l1})$$

$$\langle i_1 \rangle = I_{dc}(d'_{u1} - d'_{l1})$$



CSI Modulation: 2nd Requirement – Continuity of DC Link Current

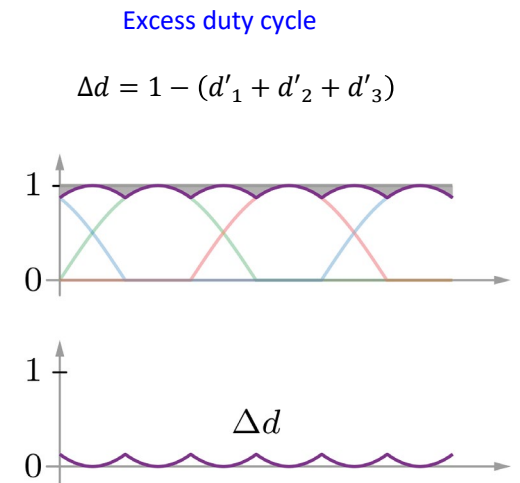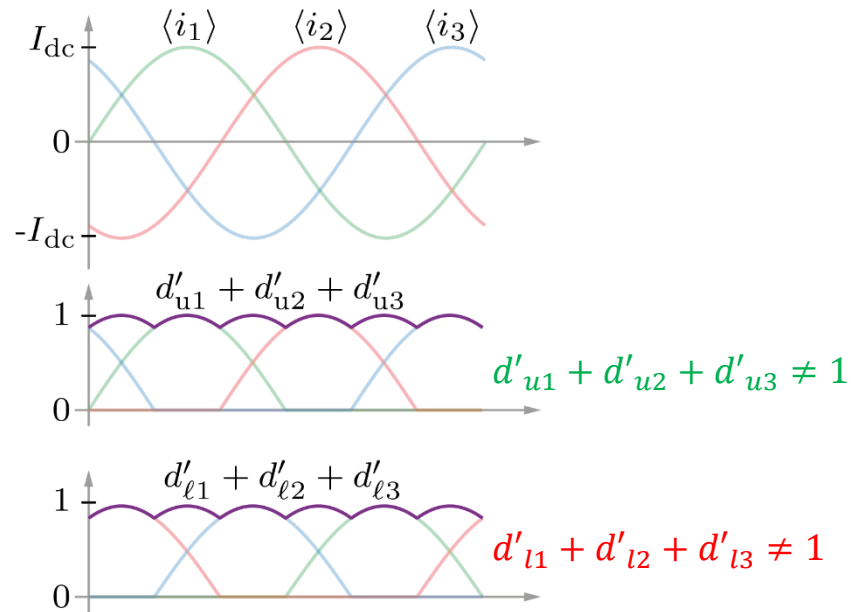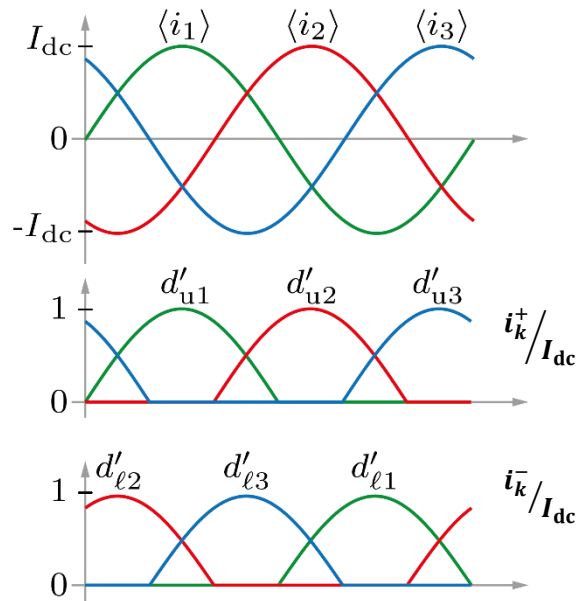- To provide the flow of the DC link current → the upper duty cycles need to sum up to unity: $\sum d_u = 1$
- To provide the flow of the DC link current → the lower duty cycles need to sum up to unity: $\sum d_l = 1$
- But, by just calculating duty cycles from the ratio i_k^+/I_{dc} of i_k^-/I_{dc} , they do not add up to unity!



- The 'leftover' duty cycle, i.e., the difference of the duty cycle sum to 1 → excess duty cycle Δd

CSI Modulation: Excess Duty Cycle - Δd


- What would happen if we distribute Δd equally between the phases \rightarrow we solve the continuity of the DC link current requirement!

$$\left. \begin{aligned} d_{u1} &= d'_{u1} + \frac{\Delta d}{3} \\ d_{u2} &= d'_{u2} + \frac{\Delta d}{3} \\ d_{u3} &= d'_{u3} + \frac{\Delta d}{3} \end{aligned} \right\} \Rightarrow d_{u1} + d_{u2} + d_{u3} = 1$$


$$\left. \begin{aligned} d_{l1} &= d'_{l1} + \frac{\Delta d}{3} \\ d_{l2} &= d'_{l2} + \frac{\Delta d}{3} \\ d_{l3} &= d'_{l3} + \frac{\Delta d}{3} \end{aligned} \right\} \Rightarrow d_{l1} + d_{l2} + d_{l3} = 1$$

Excess duty cycle

$$\Delta d = 1 - (d'_1 + d'_2 + d'_3)$$

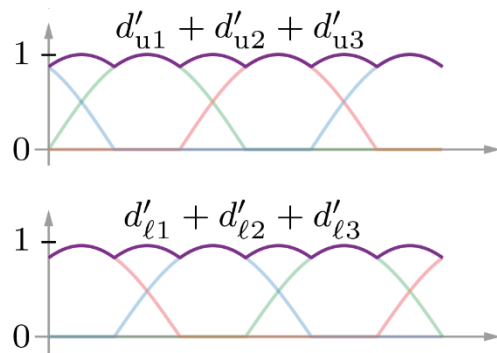

$$+ \frac{\Delta d}{3}$$

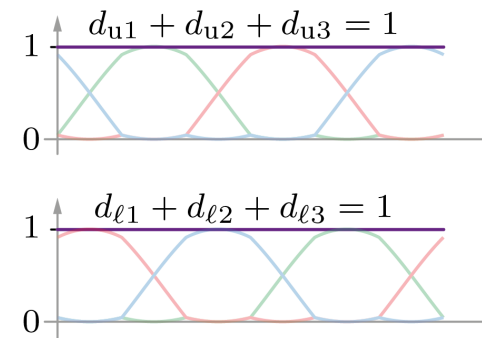

CSI Modulation: Excess Duty Cycle - Δd

- Adding excess duty cycles solve the issue of the DC link current continuity (1st req.), but did it mess up our averaged phase current (2nd req.)

$$\left. \begin{aligned} d_{u1} &= d'_{u1} + \frac{\Delta d}{3} \\ d_{u2} &= d'_{u2} + \frac{\Delta d}{3} \\ d_{u3} &= d'_{u3} + \frac{\Delta d}{3} \end{aligned} \right\} \Rightarrow d_{u1} + d_{u2} + d_{u3} = 1$$

$$\left. \begin{aligned} d_{l1} &= d'_{l1} + \frac{\Delta d}{3} \\ d_{l2} &= d'_{l2} + \frac{\Delta d}{3} \\ d_{l3} &= d'_{l3} + \frac{\Delta d}{3} \end{aligned} \right\} \Rightarrow d_{l1} + d_{l2} + d_{l3} = 1$$

$$d'_{u1} - d'_{l1} = \left(d'_{u1} + \frac{\Delta d}{3}\right) - \left(d'_{l1} + \frac{\Delta d}{3}\right) = d_{u1} - d_{l1}$$


$$\langle i_1 \rangle = I_{dc}(d_{u1} - d_{l1})$$

$$d'_{u2} - d'_{l2} = \left(d'_{u2} + \frac{\Delta d}{3}\right) - \left(d'_{l2} + \frac{\Delta d}{3}\right) = d_{u2} - d_{l2}$$

$$\langle i_2 \rangle = I_{dc}(d_{u2} - d_{l2})$$

$$d'_{u3} - d'_{l3} = \left(d'_{u3} + \frac{\Delta d}{3}\right) - \left(d'_{l3} + \frac{\Delta d}{3}\right) = d_{u3} - d_{l3}$$
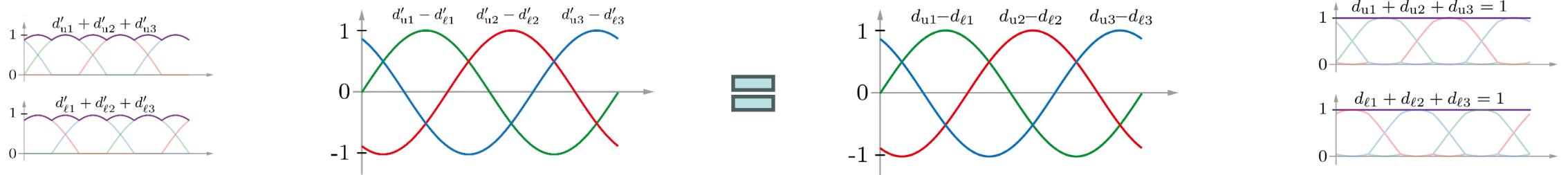
$$\langle i_3 \rangle = I_{dc}(d_{u3} - d_{l3})$$









- Adding excess duty cycle does not mess up our 2nd requirement for the averaged phase current!



CSI Modulation: 4 Simple Steps


Split calculation of the CSI duty cycle into simple steps:

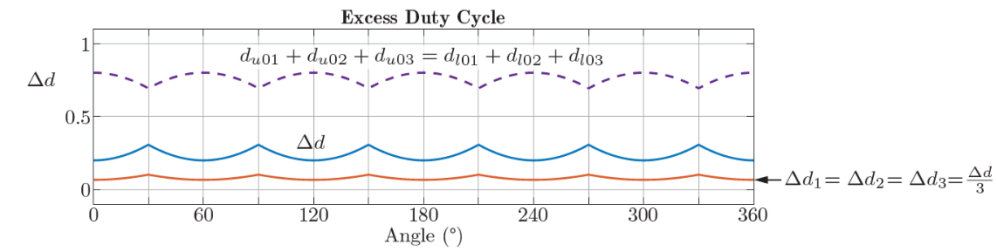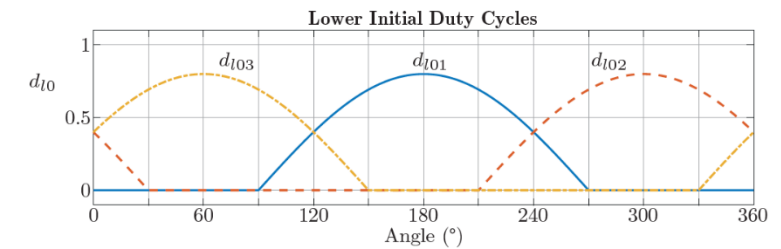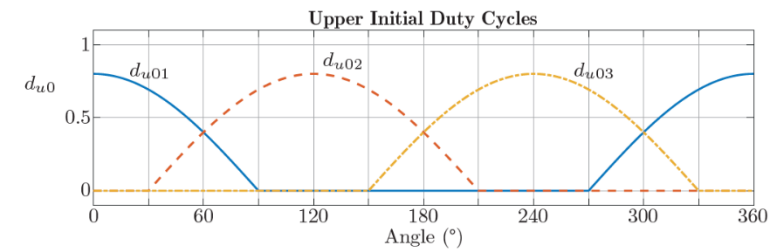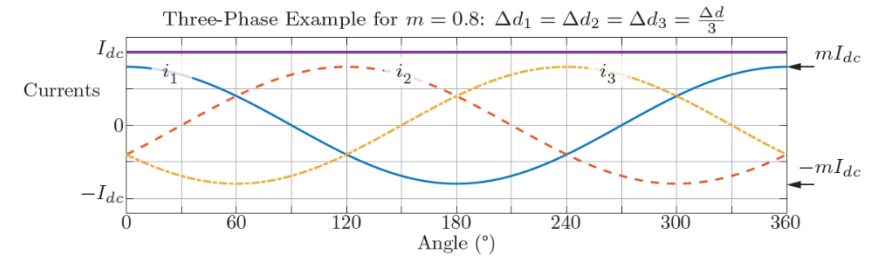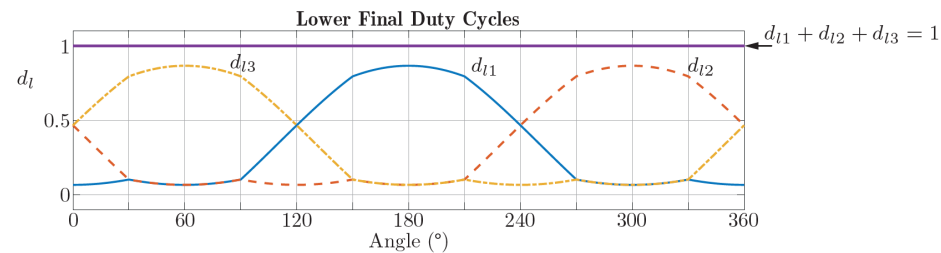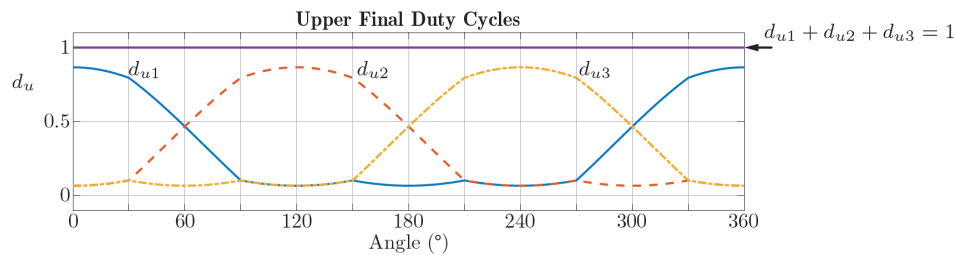1. Calculate the **initial** duty cycles as: $d_{u0k} = \frac{i_k^+}{I_{dc}}$, $d_{l0k} = \frac{i_k^-}{I_{dc}}$ where $k \in \{1,2,3\}$
2. Calculate **excess** duty cycle: $\Delta d = 1 - (d_{u01} + d_{u02} + d_{u03}) = 1 - (d_{l01} + d_{l02} + d_{l03})$
3. **Distribute** excess duty cycle: $\Delta d_1 = \Delta d_2 = \Delta d_3 = \frac{\Delta d}{3}$
4. Calculate **final** duty cycles: $d_{u1} = d_{u01} + \Delta d_1$, $d_{u2} = d_{u02} + \Delta d_2$, $d_{u3} = d_{u03} + \Delta d_3$
 $d_{l1} = d_{l01} + \Delta d_1$, $d_{l2} = d_{l02} + \Delta d_2$, $d_{l3} = d_{l03} + \Delta d_3$



Multiple Threshold Modulator (MTM)

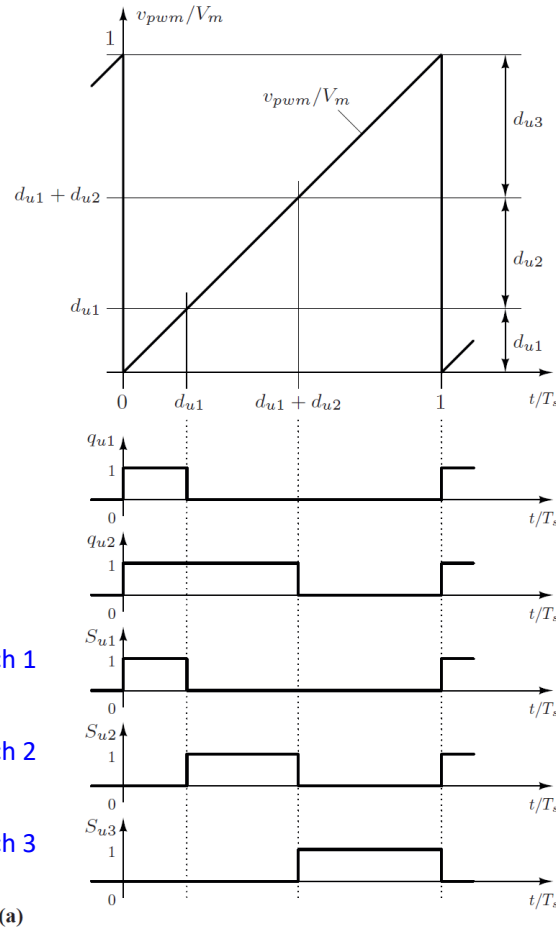- The calculated average duty cycles are supplied to the 'multiple-threshold modulator' to generate gate signals for switches




Gate signal for the upper switch 1


Gate signal for the upper switch 2

Gate signal for the upper switch 3

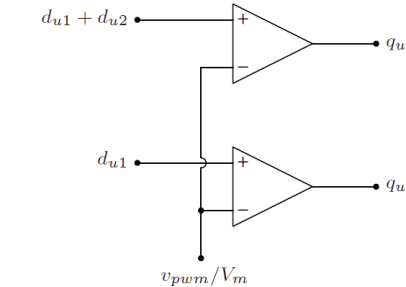Gate signals organized like 'relay race'.




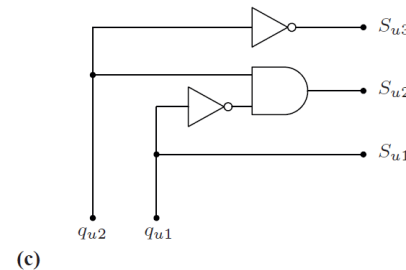
(b) and (c) are digital circuits ensuring gate signals happen one after the other ('relay race')



n -Phase CSI: the 4 Simple Steps



These modulation steps can be generalized for n -phase CSI

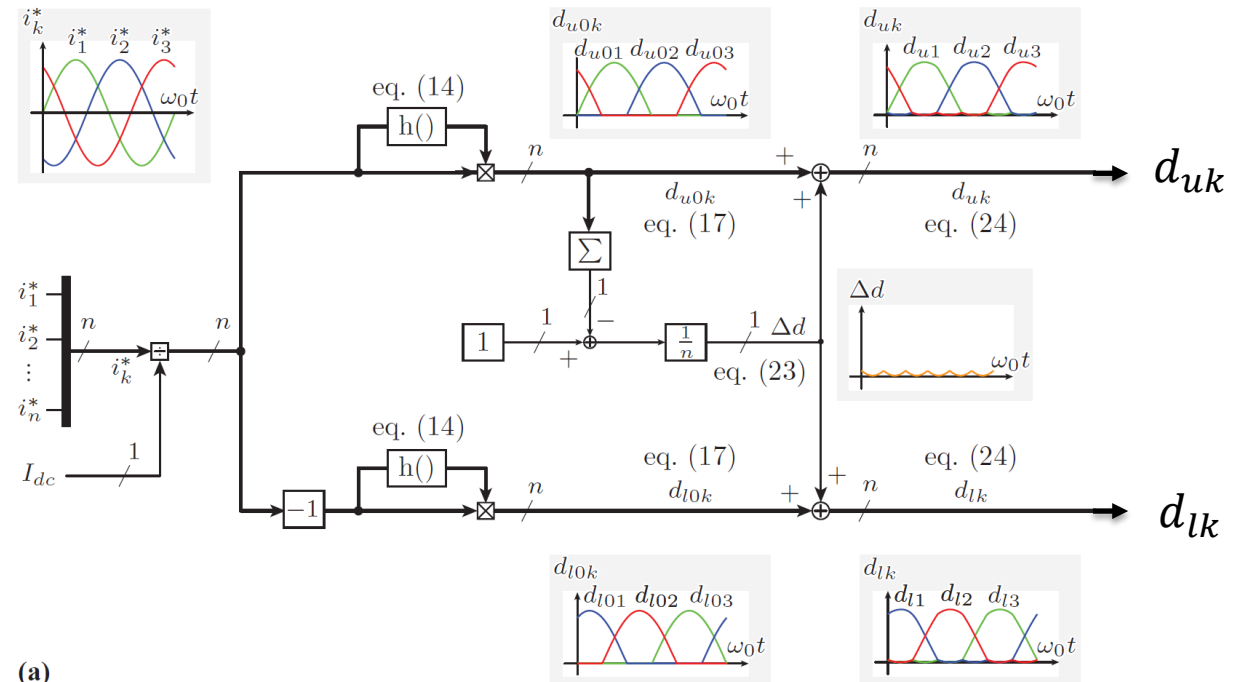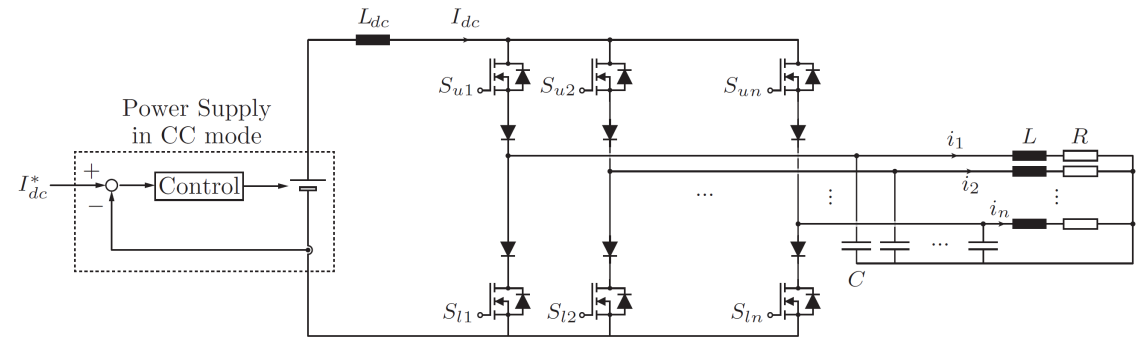1. Calculate the **initial** duty cycles as: $d_{u0k} = \frac{i_k^+}{I_{dc}}$, $d_{l0k} = \frac{i_k^-}{I_{dc}}$ where $k \in \{1, \dots, n\}$
2. Calculate **excess** duty cycle: $\Delta d = 1 - \sum_{k=1}^{k=n} d_{u0k} = 1 - \sum_{k=1}^{k=n} d_{l0k}$
3. **Distribute** excess duty cycle: $\Delta d_1 = \dots = \Delta d_n = \frac{\Delta d}{n}$
4. Calculate **final** duty cycles: $d_{uk} = d_{u0k} + \Delta d_k$
 $d_{lk} = d_{l0k} + \Delta d_k$




n -Phase CSI: the 4 Simple Steps

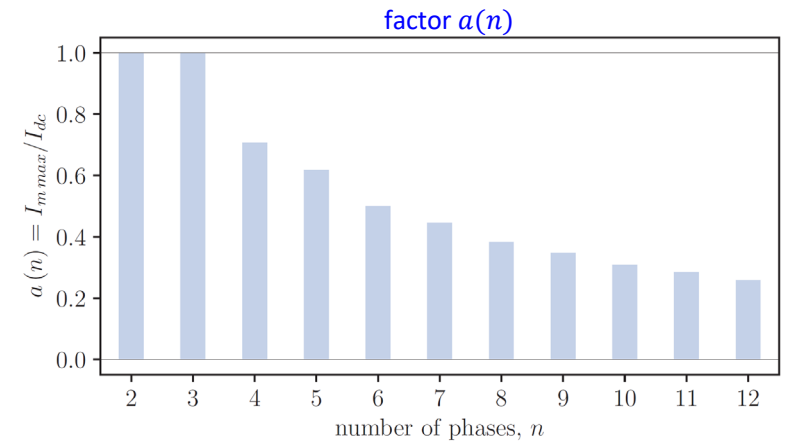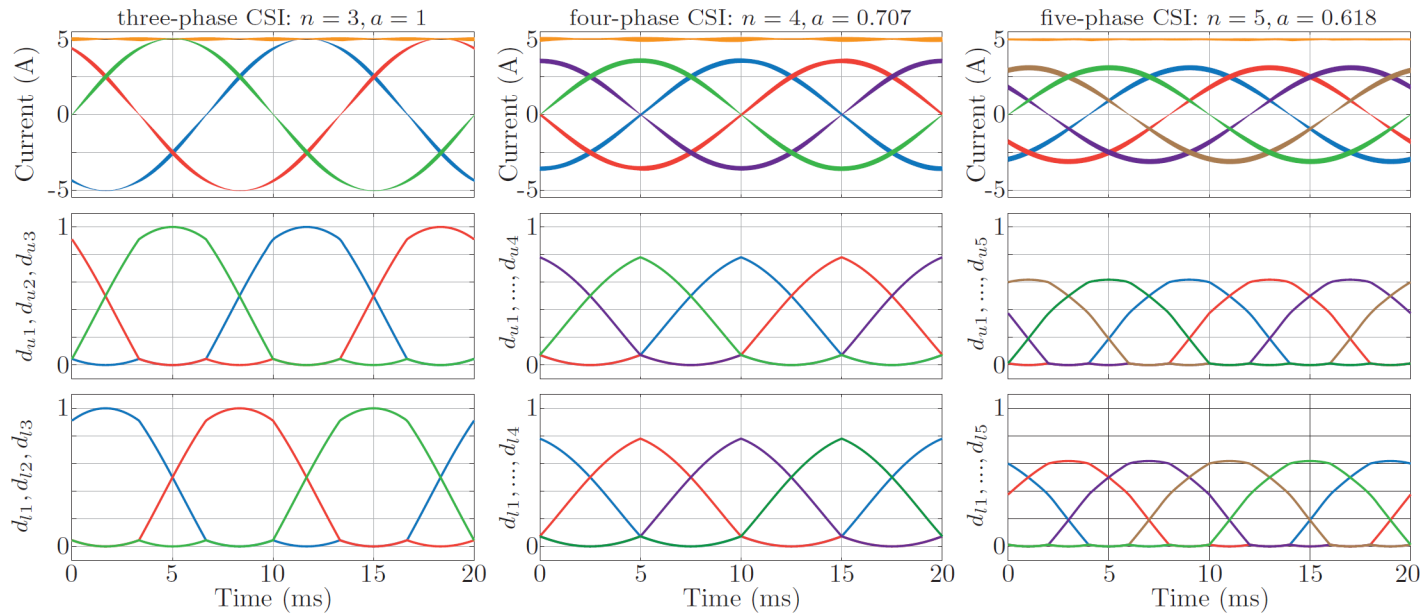- 3-, 4-, and 5-phase examples
- Phase reduction when number of phases is larger then 3 → factor a



CSI Modulation: Experimental Verification


- CSI realized using 650V SiC MOSFETs

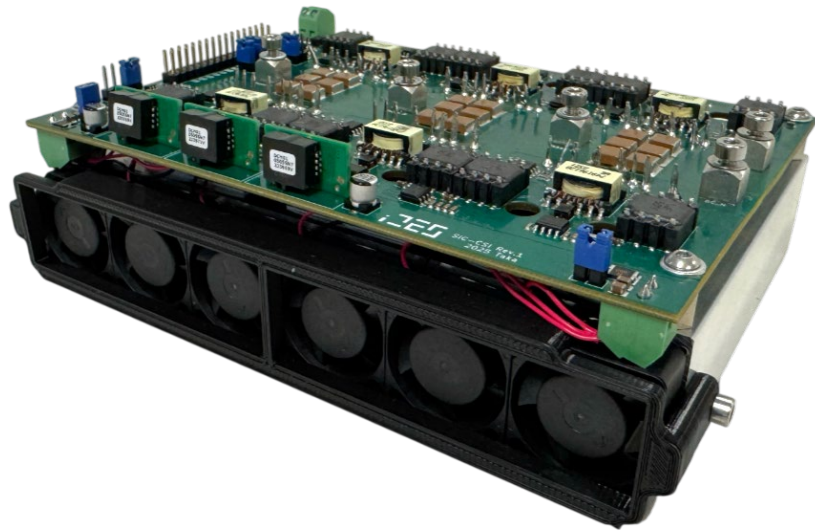

Sinusoidal reference




Arbitrary waveform

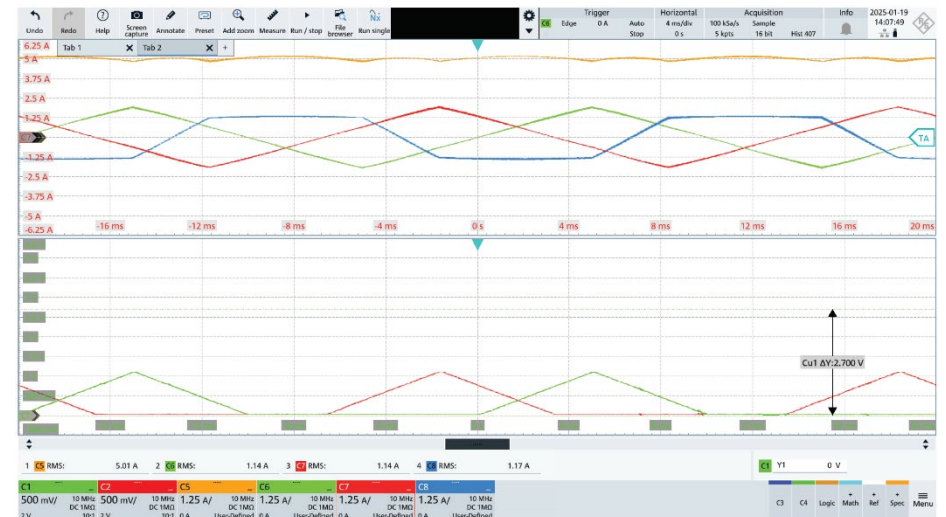


CSI Modulation: PLECS

- Reaction from PLECS for the proposed method: '...you can realize CSI modulation without C-script block? Incredible!..'


Step 1

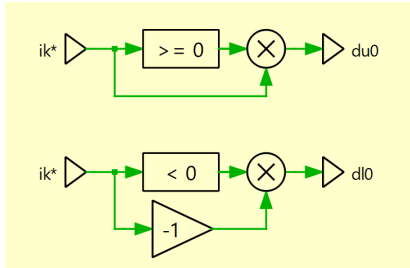


Step 2,3

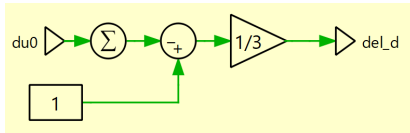

Step 4

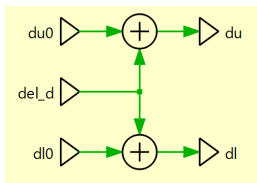

Works for any number of phases!

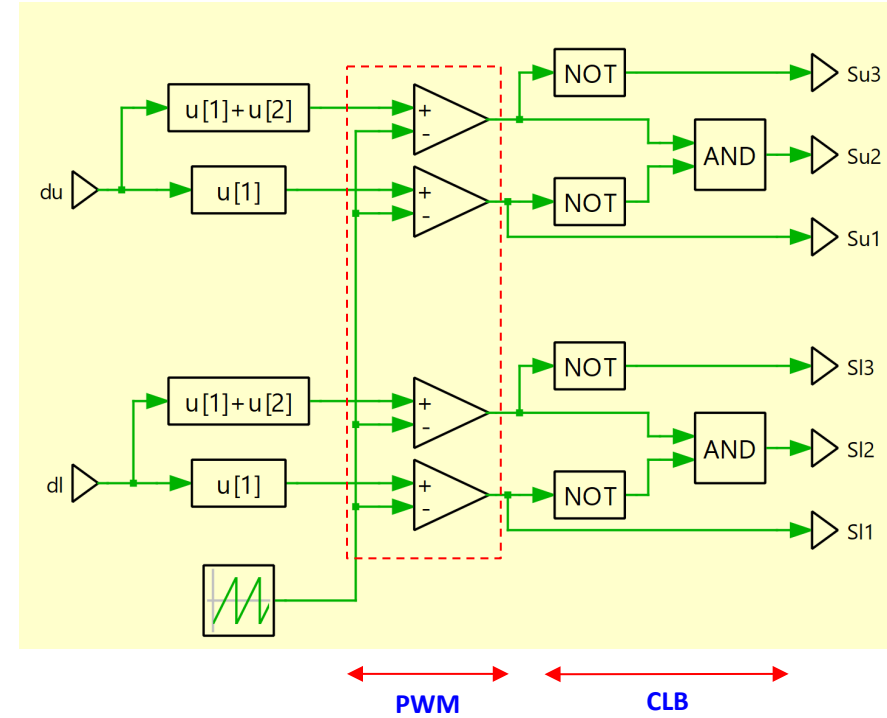


- Implementation: PWM registers + CLB (Configurable Logic Block)
- FPGA
- Infineon PSoC (old), Microchip PIC16F13145, TI F28P55x



CSI Modulation: PLECS

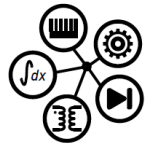- The proposed CSI modulation method will be in PLECS library in the new version 5.



PLECS

DEMO MODEL

Multi-Phase Current Source Inverter

Last updated in PLECS 5.0.1

Multi-Phase Current Source Inverter

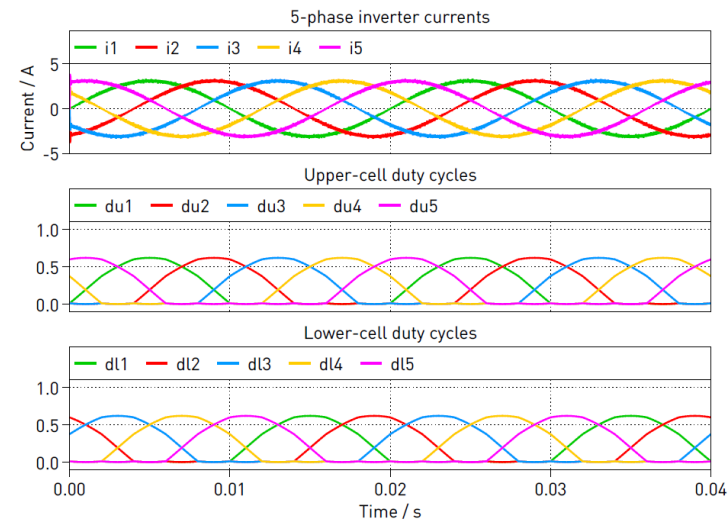


Figure 8: Simulation results for 5-phase CSI

4 Conclusion

This demo aims at showcasing a novel modulation technique for current source inverters with an arbitrary number of phases.

References

- [1] Pejović, P., Ohno, T., Borović, U. and Mirić S., "Pulse width modulation for current source inverters with arbitrary number of phases," in *Scientific Reports* 15, 8744 (2025). Available: <https://doi.org/10.1038/s41598-025-92388-9>. [Accessed: Aug. 28, 2025].




Content



- ▶ PWM Method for CSIs with Arbitrary Number of Phases
- ▶ **uniCSI: CSI Topology for Variable Reluctance Machines**
- ▶ Equivalent DC Machine (E-DCM) Concept
 - Permanent Magnet Synchronous Machines (PMSMs)
 - Variable Reluctance Machines (VRM)
- ▶ Conclusions

Reluctance Machine: Unipolar Currents

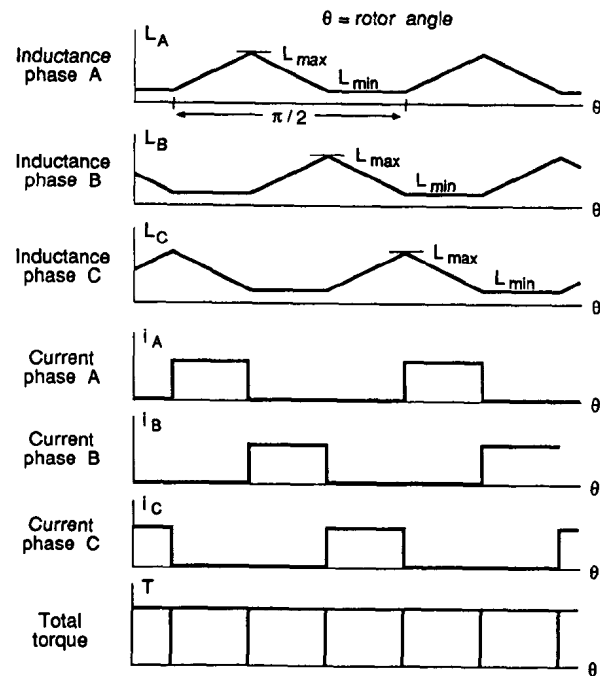- Built from iron and copper → no permanent magnets; good ratio of the torque and the moment of inertia → good acceleration
- Torque is proportional to the inductance change and the square of the current → unipolar phase currents



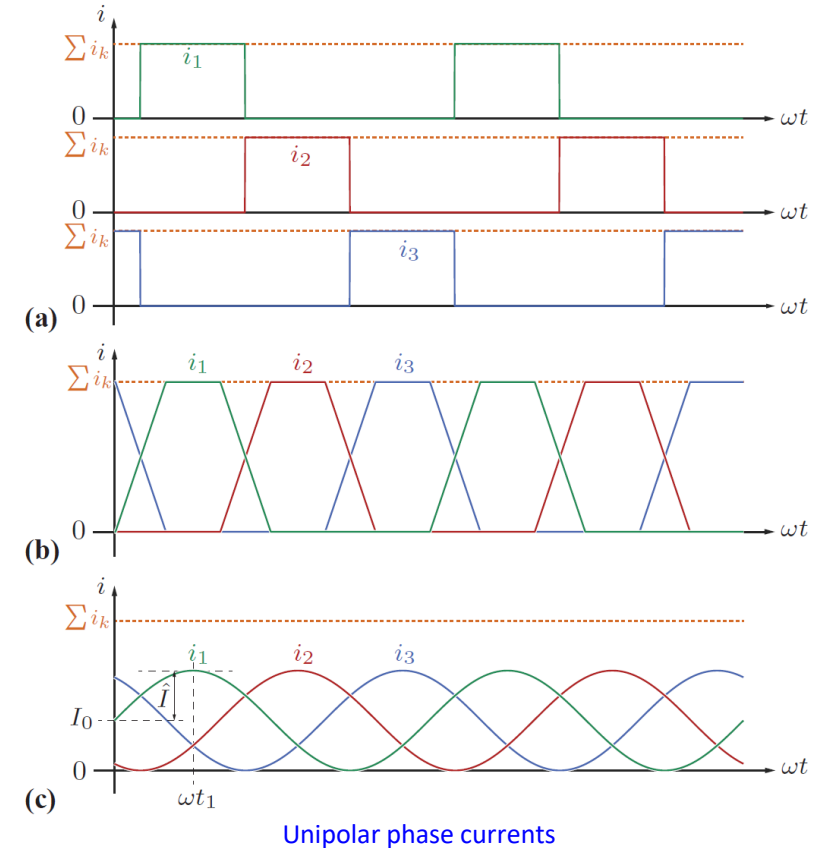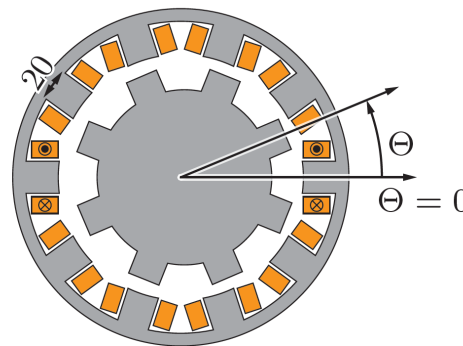
$$T \sim i^2 \frac{\partial L}{\partial \theta}$$



CSI for Unipolar Currents (uniCSI): Topology Derivation (1)

- The average phase current is proportional to the duty cycle difference of the upper and lower CSI cells
- If we need positive only current → we can realize it with the upper cell only!
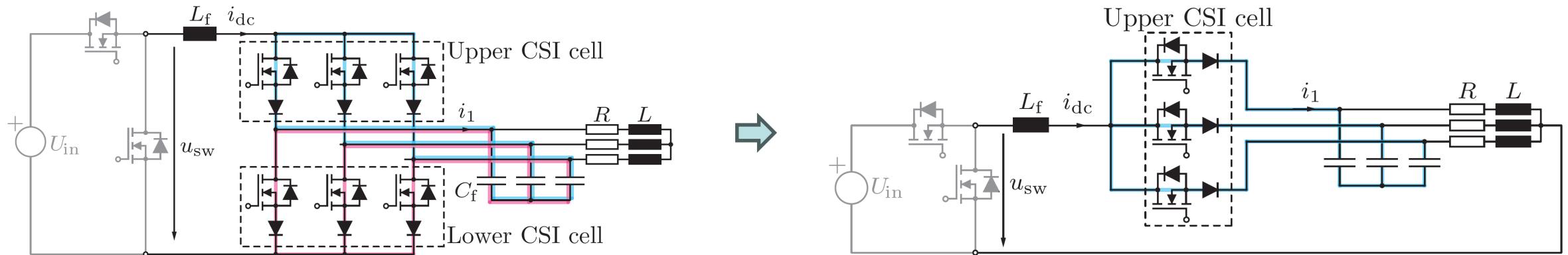
$$\langle i_1 \rangle = i_{dc}(d_{u1} - d_{l1})$$





- RL load represents a reluctance machine that needs positive only phase currents!
- How can we further develop this topology?



CSI for Unipolar Currents (uniCSI): Topology Derivation (2)

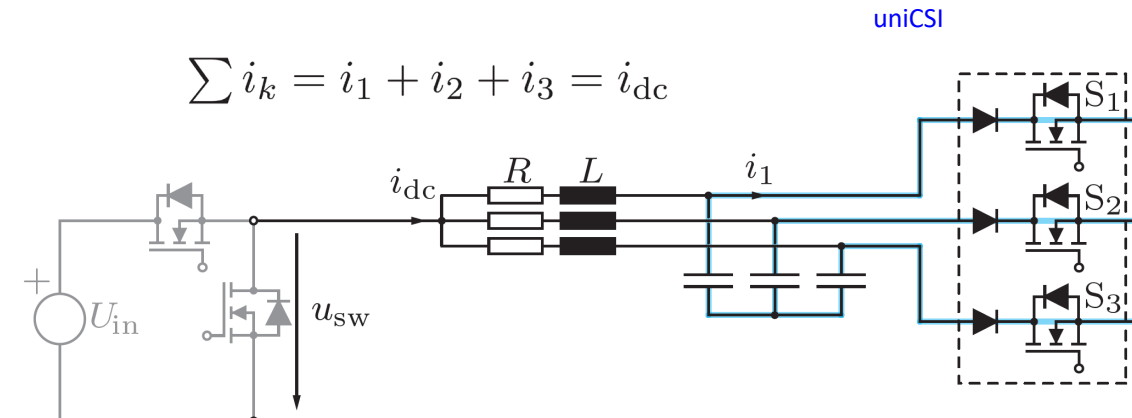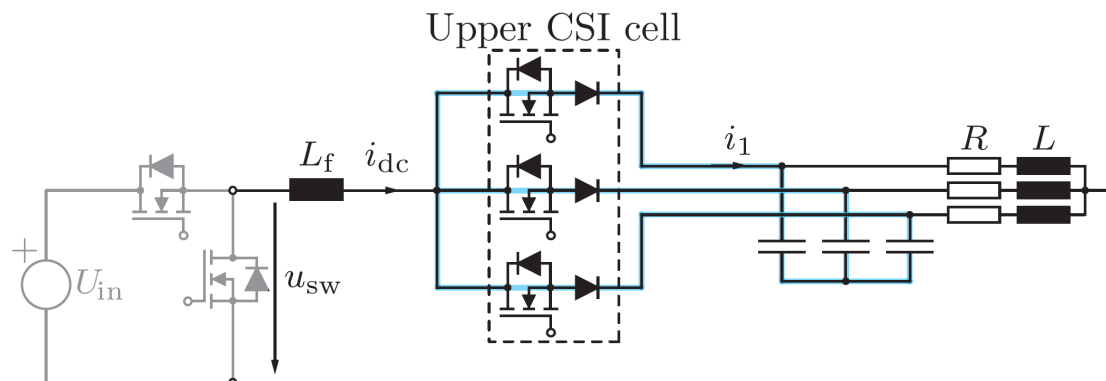- To improve the topology on the left, we can do the following:
 - Swap the position of the CSI cell and the RL load → this allows us to have MOSFETS sitting on the GND – simple gate driver design
 - We can remove the DC link inductor, since the RL load's inductance is 'seen' on the DC side and can support the CSI operation




- In uniCSI topology the sum of phase currents is equal to the DC link current.
- Open end winding of the reluctance motor → enables us to remove the DC link inductor!




uniCSI: Switch per Phase

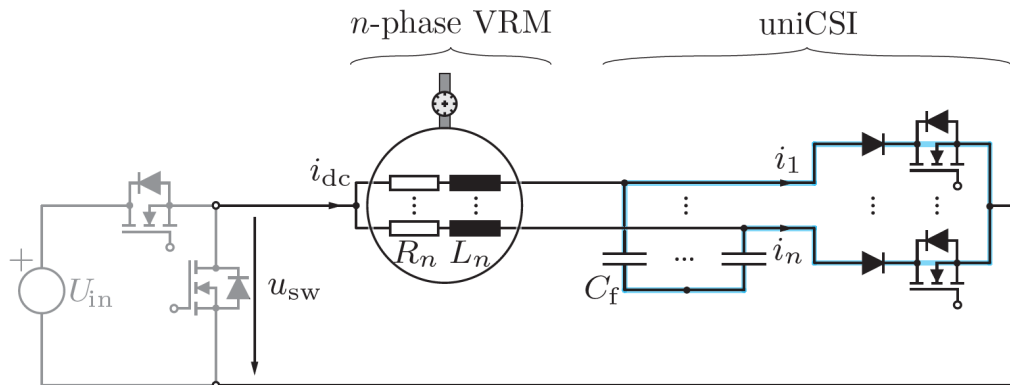
- In case of n-phase Variable Reluctance Machine (VRM), we need n-MOSFETs → switch per phase
- High-frequency operation of the switches → ‘distributing’ the DC link current among phases



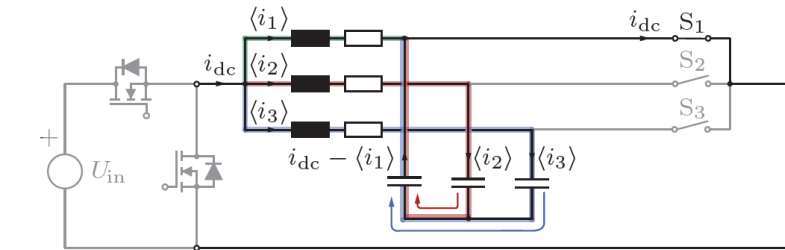
- Line to line voltages are ‘moving’ currents between phases →



(a)

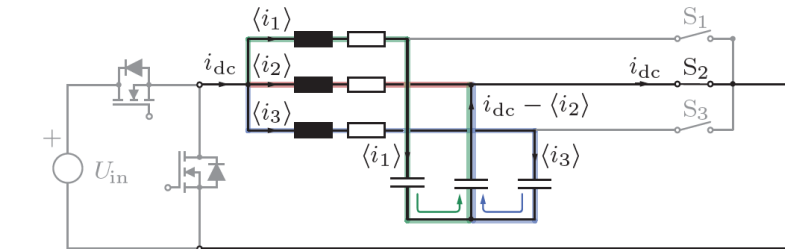

(b)

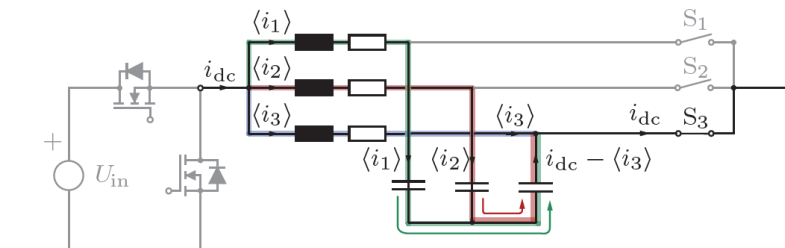


(c)


uniCSI: Simulation Results

- We can see that the line-to-line voltage are 'responsible' for moving the currents from phase to phase

Sinusoidal currents

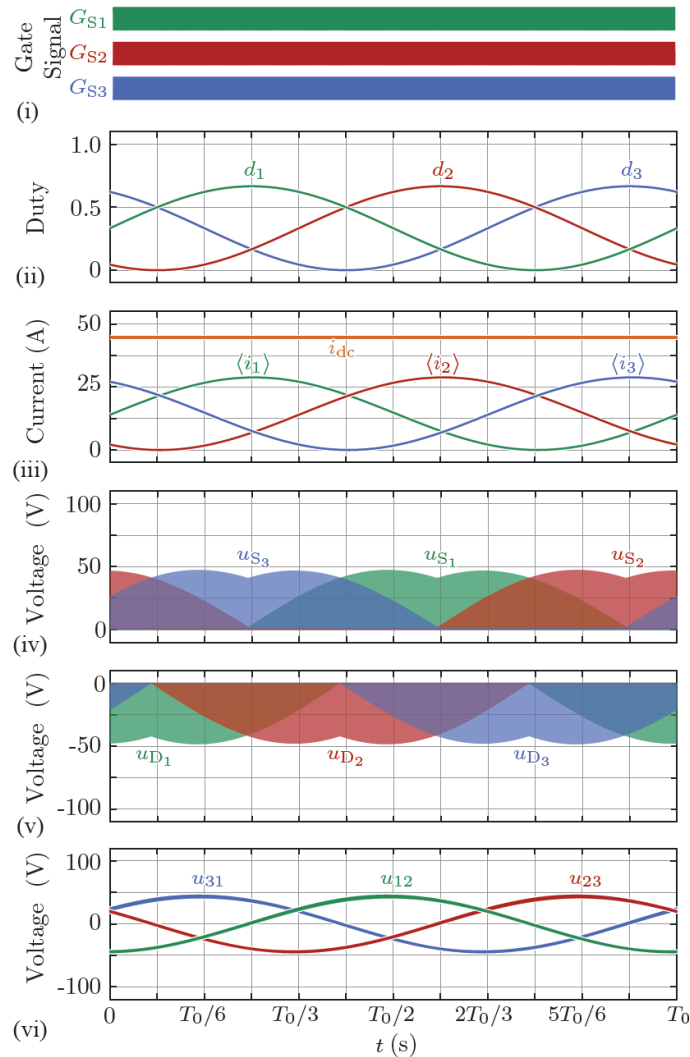

Trapezoidal currents

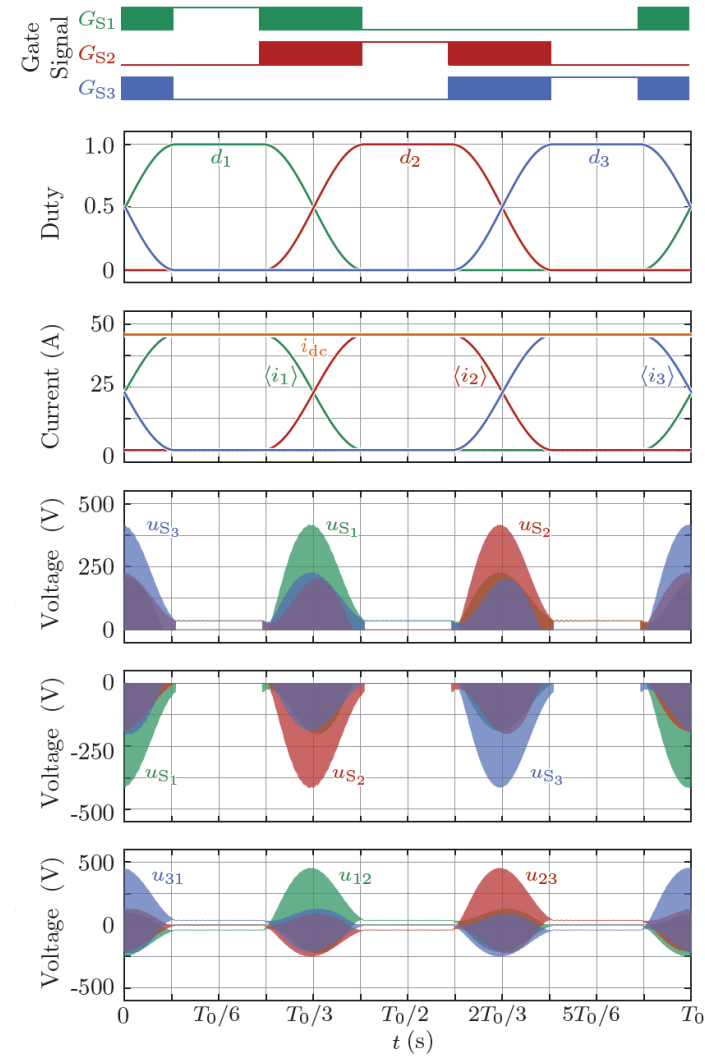




Content

- ▶ PWM Method for CSIs with Arbitrary Number of Phases
- ▶ uniCSI: CSI Topology for Variable Reluctance Machines
- ▶ **Equivalent DC Machine (E-DCM) Concept**
 - **Permanent Magnet Synchronous Machines (PMSMs)**
 - Variable Reluctance Machines (VRM)
- ▶ Conclusions



DC Industry: CSI PMSM Drive Equivalent to DC Machine

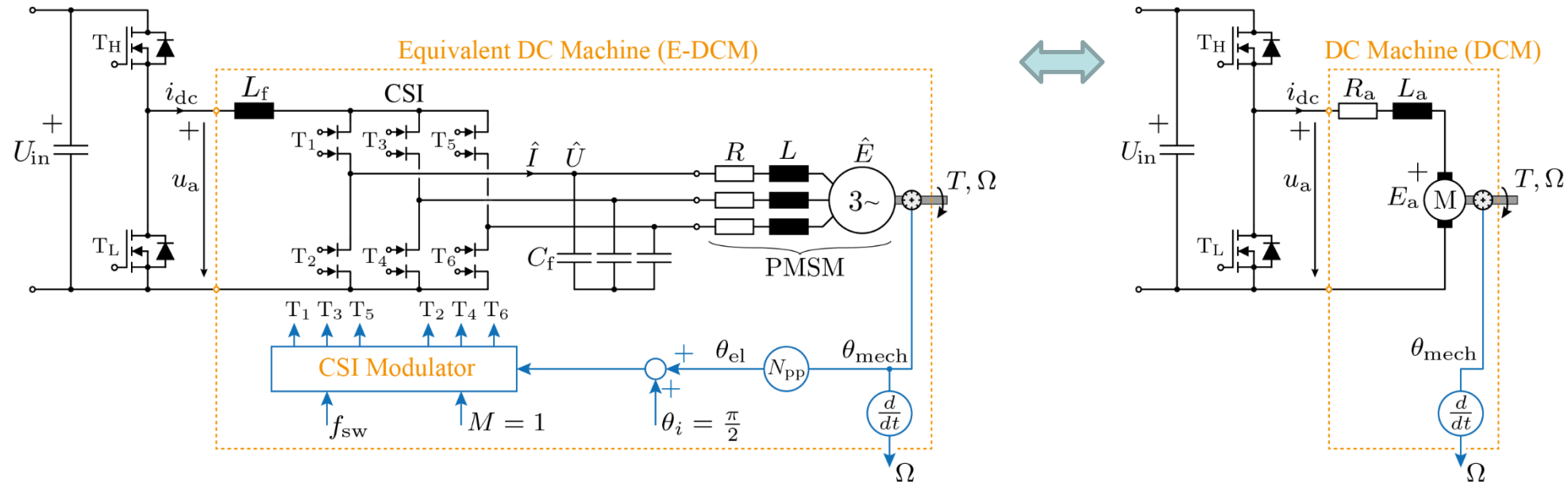
- Simplify the control of the CSI drive → mimics the CSI operation by fixing the modulation index of the CSI to $M = 1$
- 'CSI Modulator' block alternates the phase currents according to the angle information provided by the encoder



- Fixed modulation index of the CSI → DC side of the CSI is equivalent to the DC machine armature
- The torque on the PMSM shaft → directly proportional to the DC link current
- This arrangement allows us to manage the torque&speed control with the input DC-DC converter, like for a DC machine
- The user does not have to 'deal with' the CSI → enabling faster spread of CSIs in drive systems

E-DCM Speed Control Drive System

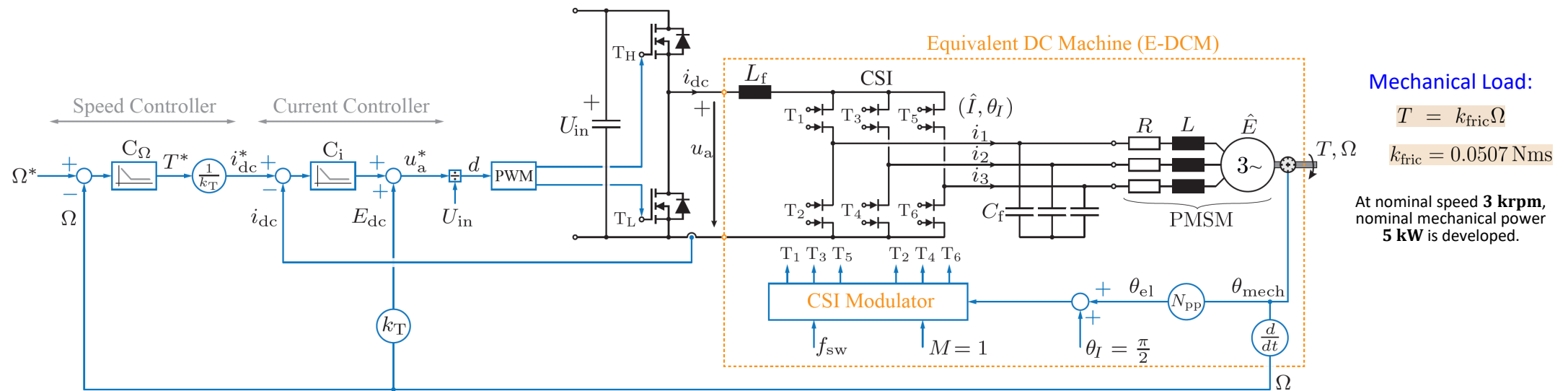- With E-DCM concept → torque on the PMSM shaft managed by the DC link current
- Cascaded control system structure → Outer speed controller loop (0.8kHz), and inner current controller loop (4kHz)






- The DC link current reference directly calculated from the speed controller torque reference: $i_{\text{dc}}^* = \frac{T^*}{k_T}$
- For tuning the current controller, the sum of the DC link inductance L_f and the DC-side equivalent inductance L_{dc} are considered: $L_f + L_{\text{dc}}$
- The user has manage only the 'DC-side' like for a DC machine

$$L_{\text{dc}} = \frac{3}{2} M^2 L = \frac{3}{2} L$$

Simulation Results: E-DCM Speed Control

- Step speed reference of 3krpm → speed controller applies the maximum possible torque during the acceleration (max. i_{dc} current of 30A)
- CSI modulation index and current angle are constant $M = 1$ and $\theta_I = \frac{\pi}{2}$

$$n_{mech} = \Omega \frac{30}{\pi}$$

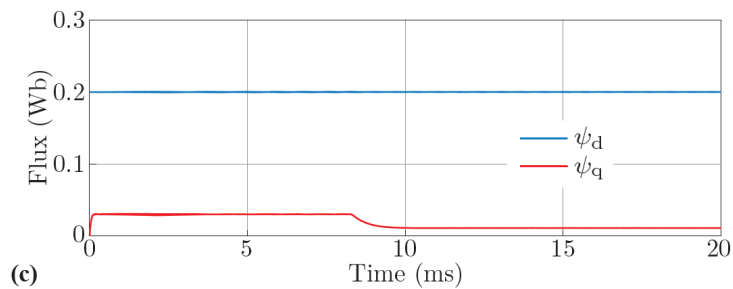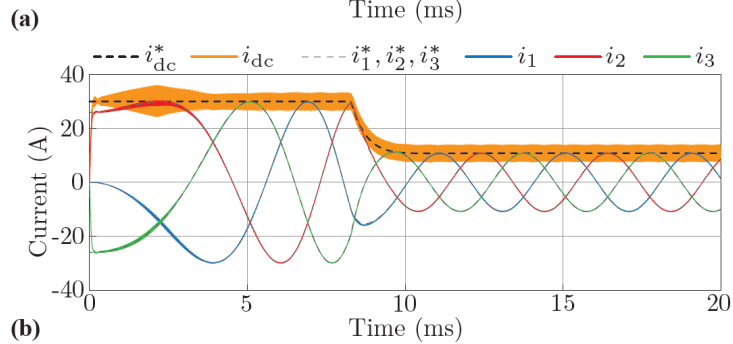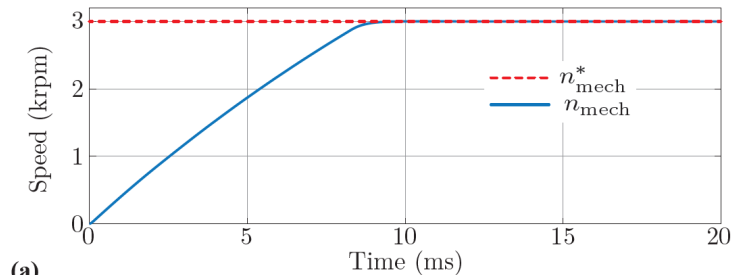



Parameter	Symbol	Value
Buck		
Input voltage	U_{in}	800 V
Switching frequency	$f_{sw,b}$	80 kHz
CSI		
DC link inductance	L_f	450 μ H
Output capacitance	C_f	0.1 μ F
Switching frequency	f_{sw}	140 kHz
Max. DC link current	$I_{dc,max}$	30 A
PMSM		
Phase resistance	R	0.2 Ω
Phase inductance	L	1 mH
Number of pole pairs	p	5
Flux linkage	Ψ	0.2 Wb
Moment of inertia	J	0.001 kgm ²
Nominal mech. power	P_{mech}	5 kW
Nominal mech. speed	n_{mech}	3000 rpm
Controller gains		
C_i closed-loop bandwidth	f_{cc}	4 kHz
C_i proportional gain	K_{pc}	49 V/A
C_i integral gain	K_{ic}	10 000 V/(As)
C_Ω cross-over frequency	f_{cs}	0.8 kHz
C_Ω proportional gain	K_{ps}	3.3 sNm
C_Ω integral gain	K_{is}	3400 Nm

→ From PMSM flux linkage we can verify that the DC link current has the effect of the torque generating quadrature current, as it impacts only the ψ_q .



DC Industry: E-DCM for PMSM-Integrated CSI

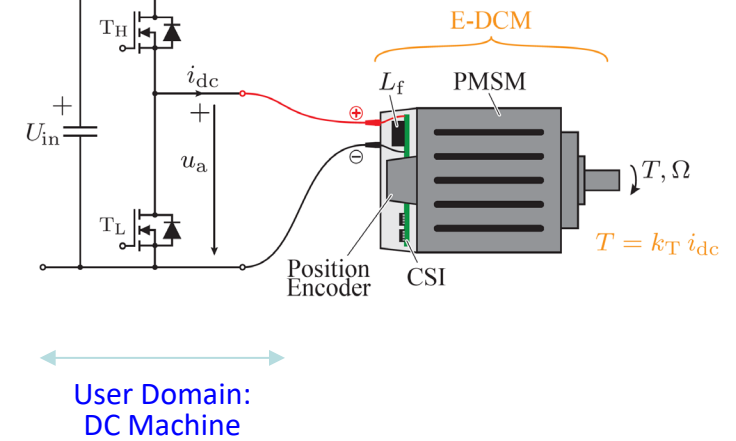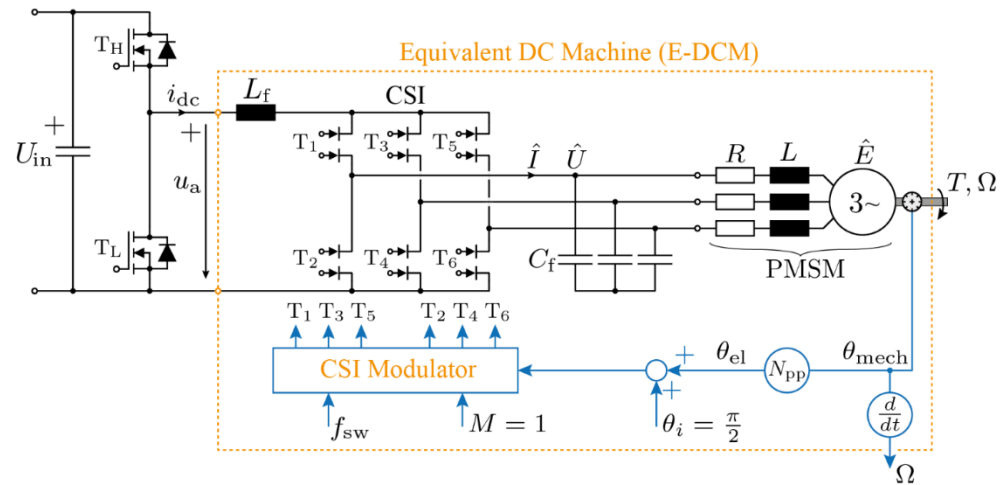- Integration of **CSI** together with **encoder** into the **PMSM** case → CSI can be run in open-loop to achieve E-DCM
- For the user the PMSM with integrated CSI appears like a DC machine if E-DCM is used



- An opportunity for **'plug-and-play'** CSI drive system → enabling **wide adoption** of CSI drive systems into various applications!




Content



- ▶ PWM Method for CSIs with Arbitrary Number of Phases
- ▶ uniCSI: CSI Topology for Variable Reluctance Machines
- ▶ **Equivalent DC Machine (E-DCM) Concept**
 - Permanent Magnet Synchronous Machines (PMSMs)
 - **Variable Reluctance Machines (VRM)**
- ▶ Conclusions

DC Industry: E-DCM for Reluctance Motors

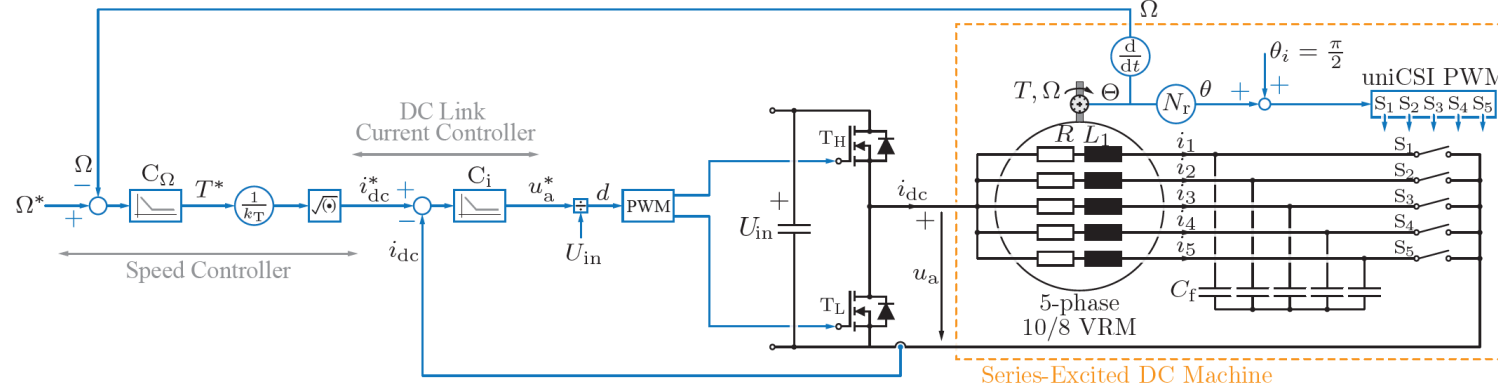- uniCSI can make reluctance machine behave like a DC machine → E-DCM approach



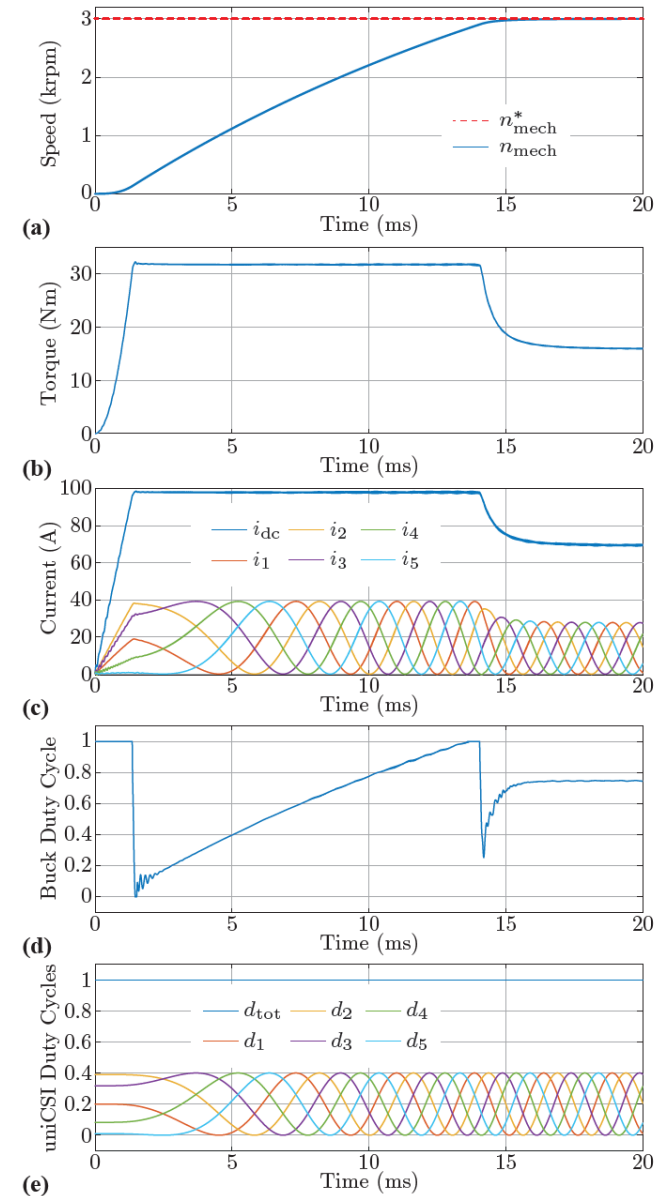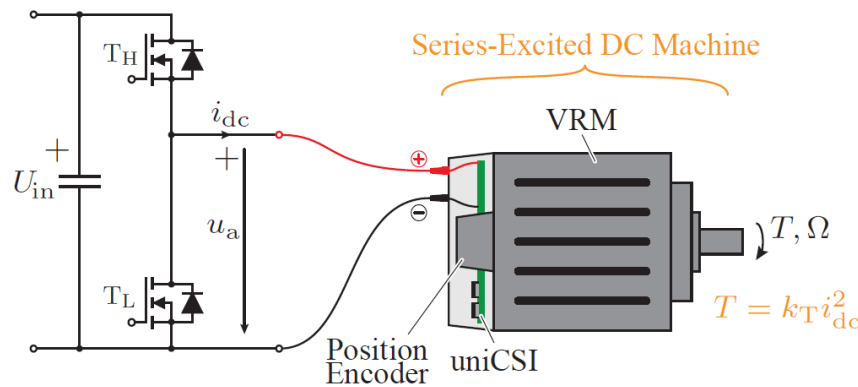- User is released of any interaction with the reluctance motor and uniCSI modulation:





Content

- ▶ PWM Method for CSIs with Arbitrary Number of Phases
- ▶ uniCSI: CSI Topology for Variable Reluctance Machines
- ▶ Equivalent DC Machine (E-DCM) Concept
 - Permanent Magnet Synchronous Machines (PMSMs)
 - Variable Reluctance Machines (VRM)
- ▶ **Conclusions**



Conclusions

- **New CSI modulation method**
 - simple PWM
 - works for any number of phases
- **New CSI topology for reluctance machines – uniCSI**
- **Equivalent DC machines for DC industry – no AC machines in the future?**



PLECS
DEMO MODEL

Multi-Phase Current Source Inverter

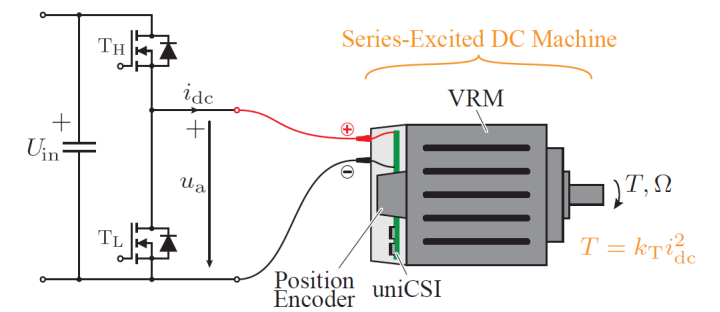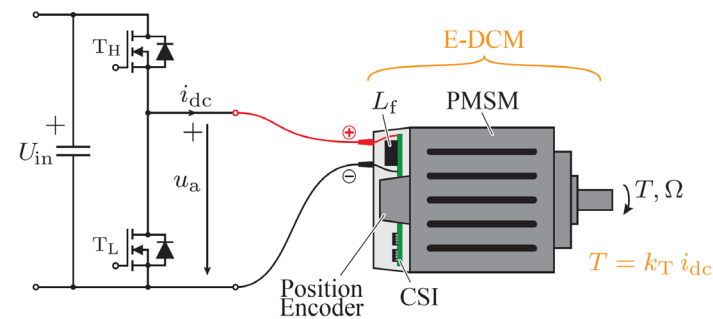

Thank you!

